

NAME \_\_\_\_\_

## EGR 2201 Lab 6

# Thevenin's Theorem & Maximum Power Transfer

### OBJECTIVES:

- To measure a circuit's Thevenin-equivalent voltage and Thevenin-equivalent resistance.
- To observe variations in current, voltage, and power as a circuit's load resistance changes.
- To verify the maximum-power-transfer theorem.


### Part 1. Measuring Thevenin-Equivalent Voltage and Resistance.

1. Select the resistors shown in Data Table A. Use the multimeter to measure their resistances, and record the values in the table. **Throughout this lab, round all predicted values, measured values, and percentage errors to three significant digits.**

Data Table A: Resistor Values

Resistor I.D.	Nominal Value	Actual Value
R <sub>1</sub>	1 kΩ	
R <sub>2</sub>	6.2 kΩ	
R <sub>3</sub>	3 kΩ	
R <sub>4</sub>	1.2 kΩ	

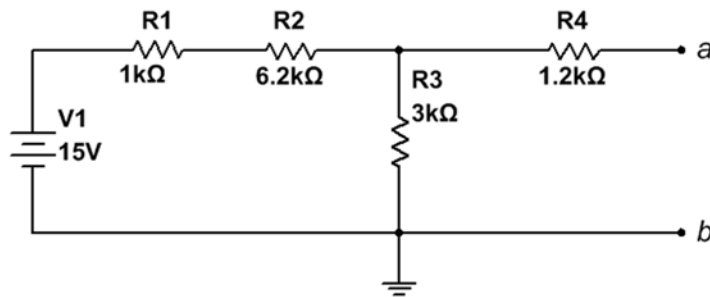
2. **Don't make any measurements until you read through step 4.** Consider the circuit shown below. Using the procedure you learned in class, predict the Thevenin-equivalent voltage  $V_{Th}$  and the Thevenin-equivalent resistance  $R_{Th}$  at the two open terminals labeled  $a$  and  $b$ . Record these values in the "Predicted" column of Data Table B. **Don't make any measurements until you read the next two steps.**



Data Table B: Thevenin-Equivalent Voltage and Resistance

Quantity	Predicted Value	Measured Value	% Error
$V_{Th}$			
$R_{Th}$			

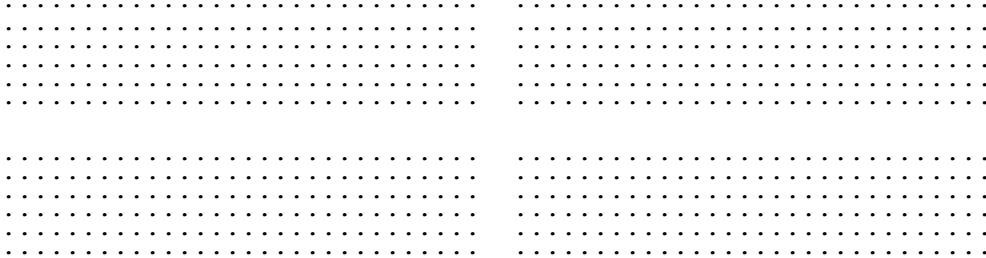- On the blank breadboard diagram below, draw resistors (**in pencil**) showing how to build the circuit. Label the resistors as R1, R2, R3, and R4. Also show the points where the + and – terminals of the 15-V source attach to the circuit, and clearly identify the points *a* and *b*.




- Now build the circuit on a breadboard.
  - To measure  $V_{TH}$ , simply measure the voltage between points *a* and *b*, with the red meter lead at point *a*.
  - To measure  $R_{TH}$ , **first turn off and disconnect the power supply**, and then replace the power supply with a short (in other words, with a wire). Then measure and record the resistance between points *a* and *b*.
 Record your measured values of  $V_{TH}$  and  $R_{TH}$  in Data Table B above. Your measured values should be close to your predictions. Compute and record percentage errors.

- Call me over so that I can check your measurements. \_\_\_\_\_

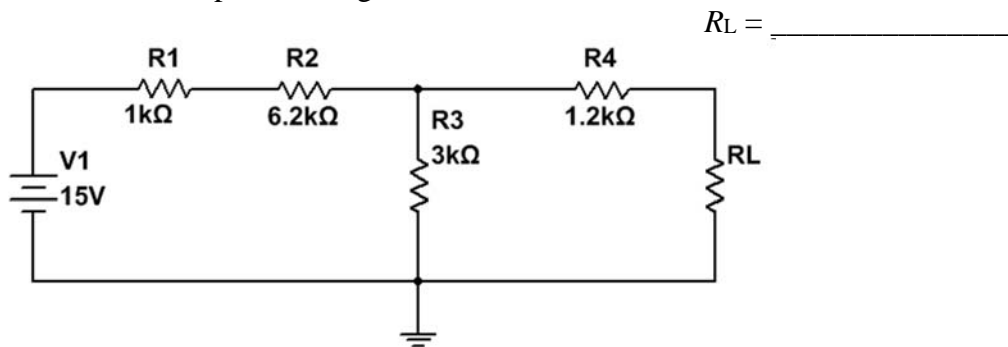**Part 2. Maximum Power Transfer.**

- Shown below is the same circuit from Part 1, but with a load resistor  $R_L$  connected across the terminals *a* and *b* that were open in the original circuit. Using your results from Part 1 and the maximum-power-transfer theorem, predict the value of  $R_L$  that will result in maximum power being transferred to  $R_L$ .



- Build the circuit on a breadboard, using your computed value of  $R_L$ .
- Measure and record the values of  $i_L$  and  $v_L$  in your circuit. From these measured values, use the power law ( $p = iv$ ) to compute the load resistor's power  $p_L$ :

Measured  $i_L =$  \_\_\_\_\_ Measured  $v_L =$  \_\_\_\_\_ Computed  $p_L =$  \_\_\_\_\_

9. Copy your values from the previous page into the middle row of Data Table C below.
10. Repeat Step 8 for four smaller values of  $R_L$  and four larger values of  $R_L$ . **Choose the smallest value to be one-tenth of the value from Step 6, and choose the largest value to be ten times the value from Step 6.** Record your values for each resistor in Data Table C, listing your resistors in order from smallest to largest.

Data Table C:  $i_L$  and  $v_L$  as  $R_L$  is Varied

	$R_L$	Measured $i_L$	Measured $v_L$	Calculated $p_L$
Smallest $R_L = 0.1 \times$ Step 6				
Values from previous page.				
Largest $R_L = 10 \times$ Step 6				

**GRAPHS** Use Microsoft Word or some other software to make the following three graphs. Give each graph a title, and label each axis with the quantity and the unit--for example, "Current (mA)." Include these graphs as part of your typed lab report.

Graph 1: Plot a graph of  $i_L$  versus  $R_L$ . (This means  $i_L$  is plotted on the vertical axis and  $R_L$  is plotted on the horizontal axis.)

Graph 2: Plot a separate graph of  $v_L$  versus  $R_L$ .

Graph 3: Plot a separate graph of  $p_L$  versus  $R_L$ .

**QUESTIONS** In your lab report, answer these questions using grammatically correct sentences.

- Using your Graph 1, describe how  $i_L$  changes as  $R_L$  increases, and explain why.
- Using your Graph 2, describe how  $v_L$  changes as  $R_L$  increases, and explain why.
- Using your Graph 3, describe how  $p_L$  changes as  $R_L$  increases, and explain why. Does your graph confirm that power is maximized for the value of  $R_L$  that you calculated in Step 6? Explain.

**LAB REPORT**

For this lab will turn in a typed lab report, with your handwritten lab sheets stapled to the back. The course syllabus has instructions on how to format your lab report, along with a sample lab report.